

• REVIEW 6 → 7:30 MONDAY NIGHT. R. T. Howe

• PS 6: DUE ON THURS. AT 4pm.



Lecture 16

ONLY ~~DO~~ DO PART
a) OF (3); (b) & (c)
→ PS 7.

- Last time:
 - MOSFET small-signal model: three (four) terminal device → complicated!
- Today :
 - Complete small-signal model: add capacitors
 - P-channel MOSFET
 - MOSFET Spice Model

Small-Signal

Putting Together a Circuit Model

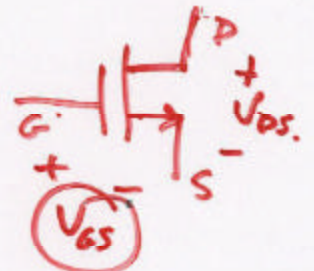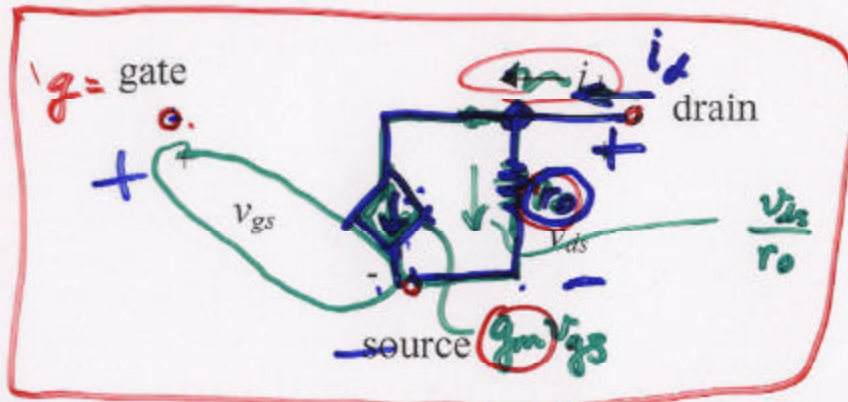


EQUATION

CIRCUIT.

Dept. of EECS

$$i_d = \frac{\partial i_D}{\partial v_{gs}} \Delta v_{gs} + \frac{\partial i_D}{\partial v_{ds}} \Delta v_{ds}$$
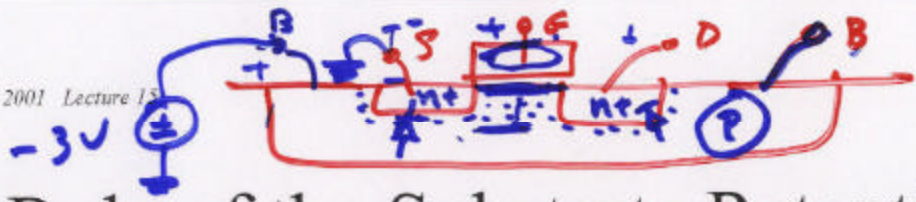
$$i_d = g_m \Delta v_{gs} + \frac{1}{r_o} \Delta v_{ds}$$



Role of the Substrate Potential

Need not be the source potential, but $V_B \leq V_S$

... COULD $V_B = V_S + \text{A LITTLE} \dots$


Effect: changes threshold voltage, which changes the drain current ... substrate acts like a "backgate"

2nd ORDER EFFECT

$$g_{mb} = \left. \frac{\Delta i_D}{\Delta v_{BS}} \right|_{(V_{GS}, V_{DS})} = \left. \frac{\partial i_D}{\partial v_{BS}} \right|_{(V_{GS}, V_{DS})}$$


V_{BS}

$$Q = (V_{GS}, V_{DS}, V_{BS})$$


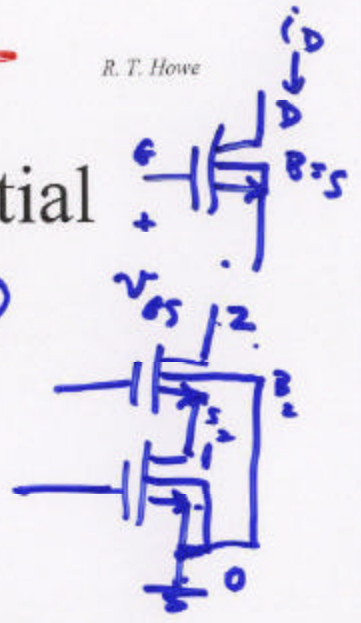


$V_{GS} < 0$
 $V_{SD} > 0$

Four-Terminal Small-Signal Model

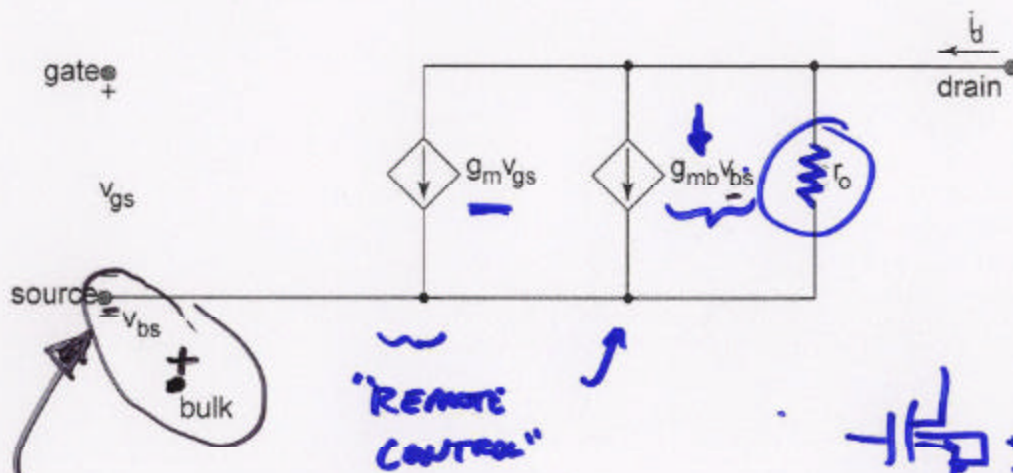


REMOTE CONTROL

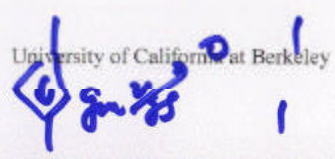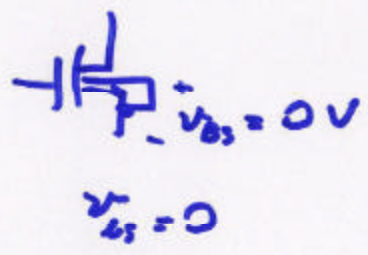

$(V_{GS} - V_{TN}) = \frac{\partial i_D}{\partial V_{TN}} \bigg|_Q = \left(\frac{W}{L} \right) \mu_n C_{ox} (V_{GS} - V_{TN}) (1 + \lambda_n V_{DS}) = \dots (V_{BS}) = g_m$

Backgate Transconductance

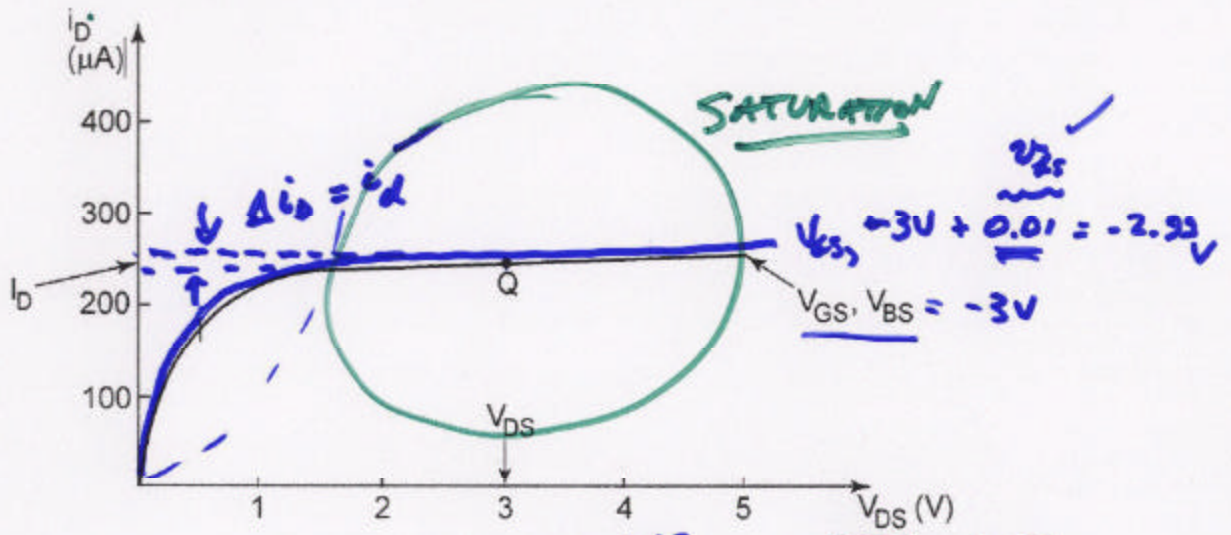

$$\text{Result: } g_{mb} = \frac{\partial i_D}{\partial v_{BS}} \bigg|_Q = \left[\frac{\partial i_D}{\partial V_{TN}} \bigg|_Q \right] \left[\frac{\partial V_{TN}}{\partial v_{BS}} \bigg|_Q \right] = r \cdot g_m$$

$\gamma \approx 0.5 \dots$

MOSFET Capacitances in Saturation

Gate-source capacitance: channel charge is not controlled by drain in saturation.

fringe electric field lines

source

gate

drain

V_{GS}

$i_D = I_G + i_G$

$R_{DS} \rightarrow \infty$

$V_{GS} = 2V$

C_{sb}

overlap L_D

overlap L_D

C_{db}

depletion region

$q_N(V_{GS})$

BACKGATE BULK

THERE IS A CHANNEL (INVERTED STATE OF MOS)

$C_g? = C_{ox} WC$

$C_g?$

$\frac{dq_N}{dV_{GS}} \dots$

Dept. of EECS

University of California at Berkeley

Gate-Source Capacitance C_{gs}

Wedge-shaped charge in saturation \rightarrow effective area is $(2/3)WL$
 (see H&S 4.5.4 for details)

$$C_{gs} = (2/3)WLC_{ox} + C_{ov}$$


OV = overlap.

LARGE (RELATIVELY)

Overlap capacitance along source edge of gate \rightarrow

$$C_{ov} = \underbrace{L_D WC_{ox}}_{A_{ov}} \dots \text{REL. SMALL. } L_D \ll L.$$

(Underestimate due to fringing fields)

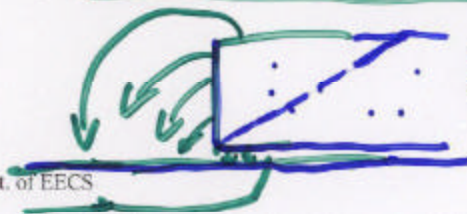

$$Z = \frac{1}{j\omega C_{gs}}$$



Gate-Drain Capacitance C_{gd}

Not due to change in inversion charge in channel


$$\frac{-\partial g_m}{\partial v_{gs}} = \phi$$

↑
SATURATION


Overlap capacitance C_{ov} between drain and source is $C_{gd} \cong L_0 W C_{ox}$

$$= W C_{gd}$$
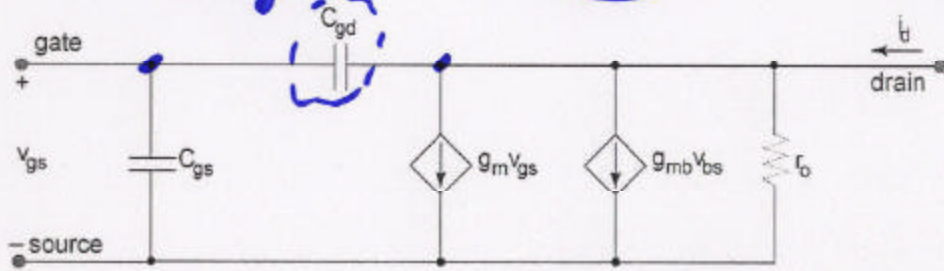
$$L_0 C_{ox} \leftarrow C_{gd} \text{ eff. } \mu\text{m.}$$




v_{bs}
+ bulk

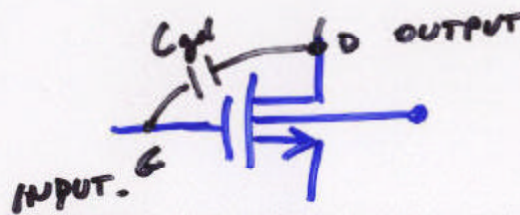

Junction Capacitances


- Drain and source diffusions have (different) junction capacitances since V_{SB} and $V_{DB} = V_{SB} + V_{DS}$ aren't the same

Complete model (without interconnects)

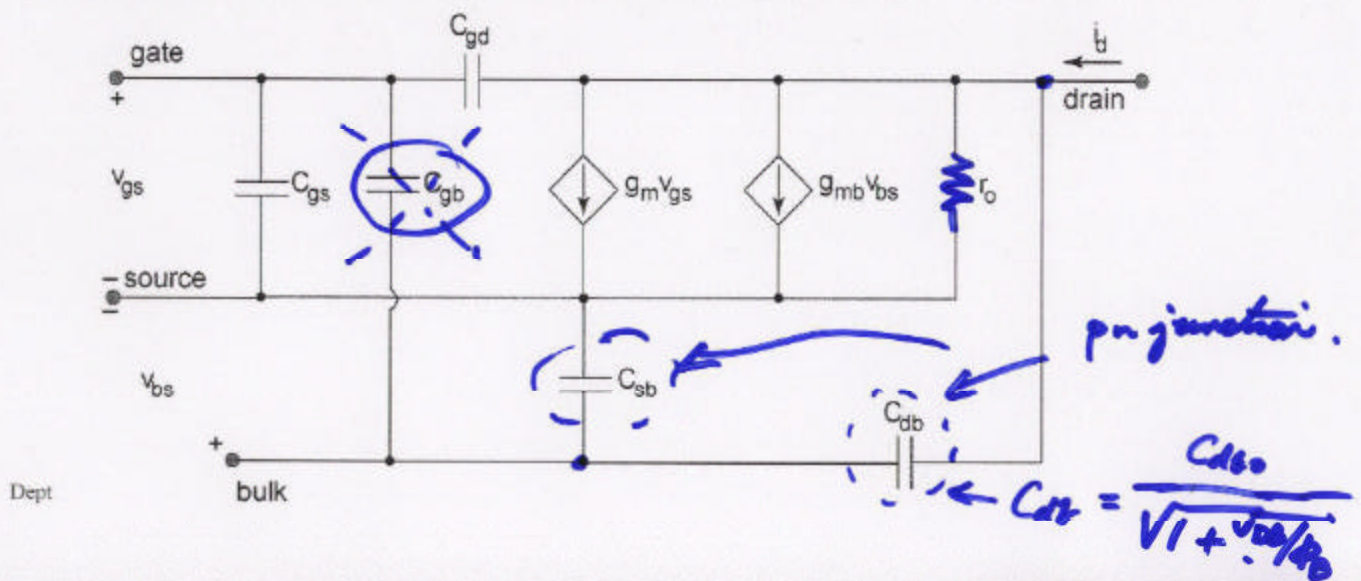


P-Channel MOSFET

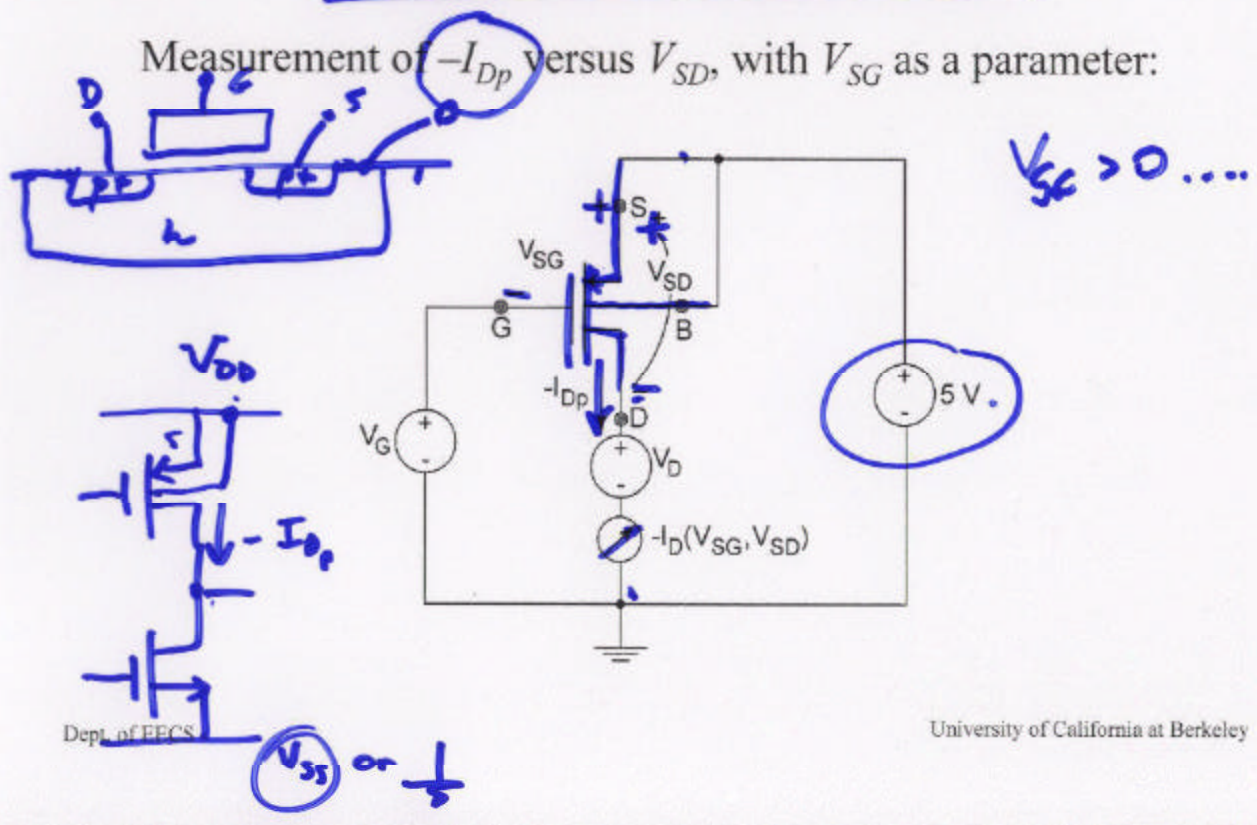Measurement of $-I_{Dp}$ versus V_{SD} , with V_{SG} as a parameter:





Square-Law PMOS Characteristics

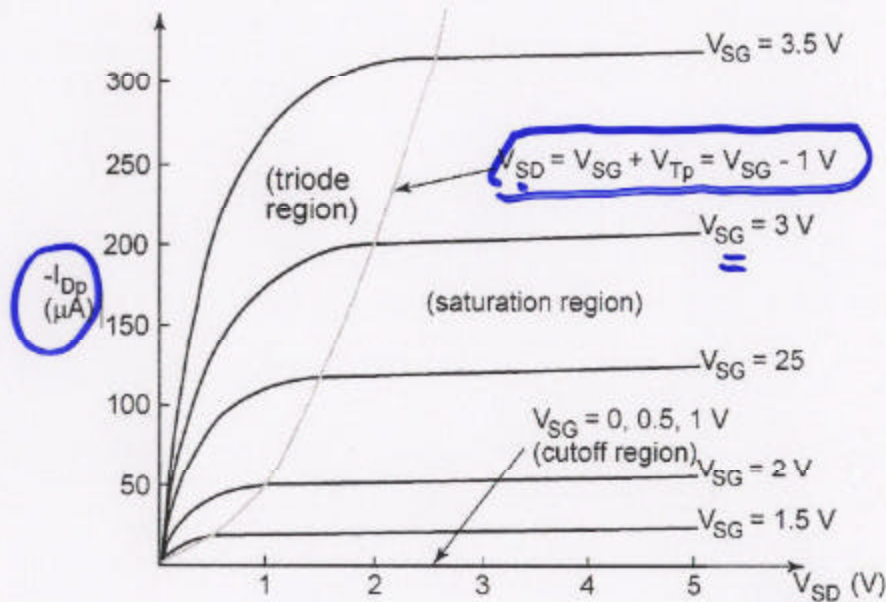


$$I_{Dp, sat} = -\left(\frac{W}{2L}\right)\mu_p C_{ox} \left(\underline{V_{SG} + V_{Tp}}\right)^2 (1 + \lambda_p V_{SD})$$

Small-Signal PMOS Model

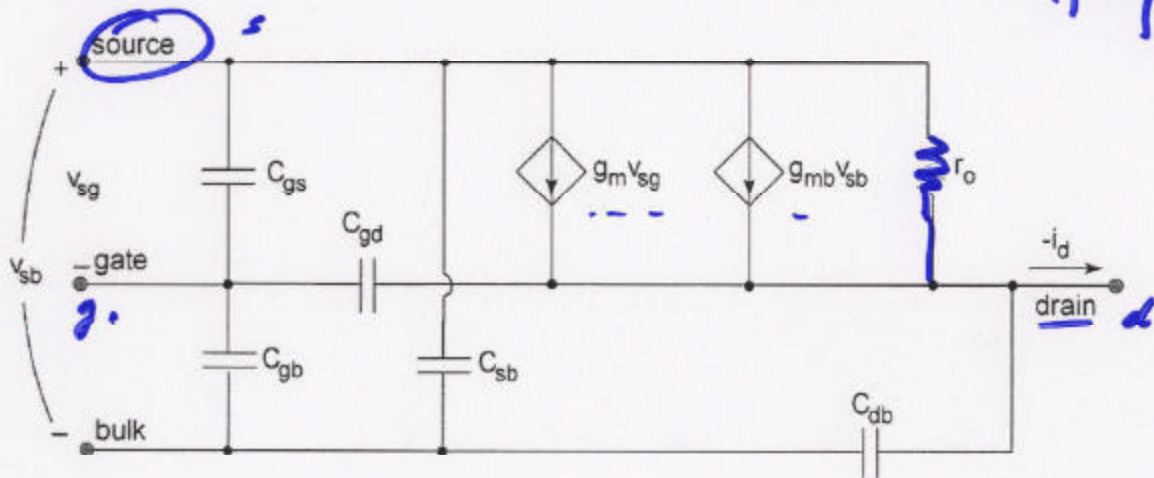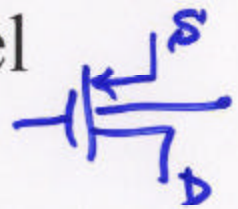
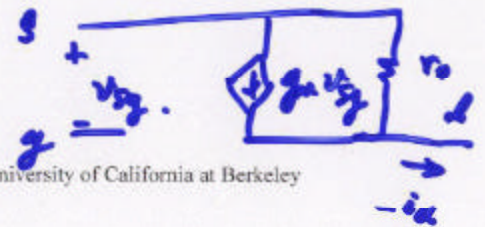
$$\frac{\partial(\quad)}{\partial V_{sg}, V_{so}, \text{ or } V_{sb}}$$



MOSFET SPICE Model

Many “levels” ... we will use the square-law
“Level 1” model

See H&S 4.6 + Spice refs. on reserve for details.

```
.MODEL MODN NMOS LEVEL = 1 VTO = 1 KP = 50U LAMBDA = .033 GAMMA = .6
+ PHI = 0.8 TOX = 1.5E-10 CGDO = 5E-10 CGSO = 5E-10 CJ = 1E-4 CJSW = 5E-10
+ MJ = 0.5 PB = 0.95
.MODEL MODP PMOS LEVEL = 1 VTO = -1 KP = 25U LAMBDA = .033 GAMMA = .6
+ PHI = 0.8 TOX = 1.5E-10 CGDO = 5E-10 CGSO = 5E-10 CJ = 3E-4 CJSW = 3.5E-10
+ MJ = 0.5 PB = 0.95
```