



NS – 617

14

I Semester B.C.A. Degree Examination, November/December 2016  
(Repeaters) (Y2K8 Scheme)  
BCA 104 : ELECTRONICS

Time : 3 Hours

Max. Marks : 70/60

**Instruction :** 60 Marks is only for those admitted prior to 2011-12.  
Section D is for those admitted from 2011-12 and onwards.

SECTION – A

I. Answer **any ten** questions. **Each** question carries **1** mark : **(1×10=10)**

- 1) State Ohm's law.
- 2) What is a bilateral network ?
- 3) Define ripple factor.
- 4) What is rms value of the ac ?
- 5) Expand VLSI.
- 6) Represent  $348_{(10)}$  in Excess – 3 code.
- 7) What is a bit ?
- 8) Write the truth table of Ex-NOR gate.
- 9) Draw the pin diagram of IC 7404.
- 10) What is sequential logic circuit ?
- 11) What is a flip-flop ?
- 12) What is forbidden state in a flip-flop ?

P.T.O.



## SECTION - B

II. Answer **any five** questions. **Each** question carries **3** marks : **(3×5=15)**

- 13) State and explain Kirchhoff's current law.
- 14) Explain the formation of n-type semiconductor.
- 15) Convert  $503_{(10)} = \text{_____}_{(2)} = \text{_____}_{(8)} = \text{_____}_{(16)}$ .
- 16) State and prove De'Morgan's theorem.
- 17) What is a half-subtractor ? Write its truth table and logic circuit.
- 18) What is AND logic gate ? Write its truth table and pin diagram of IC 7408.
- 19) Explain the working of Master-Slave flip-flop.
- 20) What is T-flip-flop ? Realise T-flip-flop using JK-flip-flop.

## SECTION - C

III. Answer **any five** questions. **Each** question carries **7** marks : **(7×5=35)**

- 21) State and explain Thevenin's theorem with necessary diagrams. 7
- 22) Write any four comparisons of conductors, insulators and semiconductors. 7
- 23) With the circuit diagram and waveforms explain the working of full-wave rectifier. Give the expression for its efficiency. 7
- 24) a) Explain the steps to subtract  $101100_{(2)}$  from  $111000_{(2)}$  using 2's complement method.
- b) Find the binary equivalent of the Gray Code 110010. (5+2)
- 25) a) Convert :

$$B4C5_{(16)} = \text{_____}_{(10)} = \text{_____}_{(8)} = \text{_____}_{(2)}$$

- b) Simplify the Boolean expression using K-map.

$$f(A, B, C, D) = \sum_m(0, 2, 6, 8, 10, 15) + \sum_d(7, 13, 14) \quad (3+4)$$



- 26) a) What is full subtracter ? Write its truth table, output expressions. Realise full subtracter using two subtracters. (6+1)  
b) What is BCD adder ?
- 27) a) Explain the working of 4-bit parallel adder. (4+3)  
b) Draw the logic circuit of 4-bit adder/subtractor using IC 7483 and IC 7486.
- 28) a) With the logic circuit and truth table, explain the operation of JK-FF. (5+2)  
b) What is a shift register ? Mention the types of shift registers.

SECTION – D

IV. Answer **any one full** question : (10x1=10)

- 29) a) State and explain maximum power transfer theorem. 5  
b) Compare these logic families DTL, TTL and CMOS. 5
- 30) a) List the properties of semiconductors. 5  
b) Write any three Boolean laws. 3  
c) Give the importance of clock in sequential circuits. 2
-