

7 Analog-Digital-Conversion

7.1 Components of A/D-Converters

Sample and hold circuit, Quantisation

7.2 Flash A/D-Converter


7.3 Iterative A/D-Converter

7.4 A/D-Converter with an Intermediate Quantity

7.5 Sigma-Delta-Converter


7.6 Errors by A/D-Converters

7.1 Components of A/D-Converters

 


7.1 Components of A/D-Converters

Sampling

 

Autliers

 

Earlier or later sampling gives a different result

7.1 Components of A/D-Converters

Sampling

$$x_a(t) = x_e(t) \sum_{k=-\infty}^{+\infty} \delta(t - kT_0)$$

Sampling Period $T_0 = \frac{1}{f_{Sampl}}$

Fourier Transformation

$$x_e(t) \xrightarrow{\bullet} X_e(\omega) = \int_{-\infty}^{\infty} x_e(t) e^{-j\omega t} dt$$

Inverse Fourier Transformation

$$x_e(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} X_e(\omega) e^{j\omega t} dt$$

Multiplication in Time Domain \rightarrow Convolution in Frequency Domain

$$x(t) u(t) \xrightarrow{\bullet} X(\omega) * U(\omega) = \int_{-\infty}^{\infty} X(\omega') U(\omega - \omega') d\omega'$$

7.1 Components of A/D-Converters

Sampling

$$x_e(t) \circlearrowright X_e(\omega)$$

$$\sum_{k=-\infty}^{+\infty} \delta(t - kT_0) \circlearrowright \frac{1}{T_0} \sum_{n=-\infty}^{\infty} \delta\left(f - \frac{n}{T_0}\right) \quad T_0 : \text{Sampling Period}$$



$$\begin{aligned} x_a(t) = x_e(t) \sum_{k=-\infty}^{+\infty} \delta(t - kT_0) &\circlearrowright X_a(f) = X_e(f) * \frac{1}{T_0} \sum_{n=-\infty}^{\infty} \delta\left[f - \frac{n}{T_0}\right] \\ &= \int_{-\infty}^{\infty} \left\{ \frac{1}{T_0} \sum_{n=-\infty}^{\infty} \delta\left[u - \frac{n}{T_0}\right] \right\} X_e(f-u) du \\ (\text{Changing Summation and Integral}) &= \frac{1}{T_0} \sum_{n=-\infty}^{\infty} \int_{-\infty}^{\infty} \delta\left[u - \frac{n}{T_0}\right] X_e(f-u) du \\ (\text{Dirac-Function}) &= \frac{1}{T_0} \sum_{n=-\infty}^{\infty} X_e\left(f - \frac{n}{T_0}\right) \end{aligned}$$

7.1 Components of A/D-Converters


Sampling

  Example Convolution


$$X(\omega) * U(\omega) = \int_{-\infty}^{\infty} X(\omega') U(\omega - \omega') d\omega'$$



Mirroring

 

Translation

 


7.1 Components of A/D-Converters


Sampling

Example Convolution

Translation

 

Multiplication

 






Integration

7.1 Components of A/D-Converters

Sampling

     Example Convolution with a Dirac Pulse


$$X(t) * \delta(t - t_0) = \int_{-\infty}^{\infty} \delta(t - t_0) \cdot X(t - \tau) d\tau = X(t - t_0)$$



7.1 Components of A/D-Converters

Sampling



Example Convolution with a Dirac Pulse

 



7.1 Components of A/D-Converters

Sampling


Time Domain

  


Frequency Domain

  

Multiplication

 


Convolution

 

7.1 Components of A/D-Converters

Sampling

 

Sampling theorem by Shannon or Nyquist-Criterion


$$f_{Sampl} > 2 f_g \quad \text{or more general} \quad f_{Sampl} > 2 (f_{\max} - f_{\min})$$

7.1 Components of A/D-Converters

Anti-aliasing-Filter

$$f > \frac{f_{Samp!}}{2} \quad \text{Pre-filtering} \quad \rightarrow \text{no overlapping!}$$

 The slow rate of the Filter should be considered!





7.1 Components of A/D-Converters

Sample & Hold Circuit

→ Signal amplitude is hold constant
during A/D-Conversion

	S_1	S_2
Step 1: Sample	closed	opened
Step 2: Hold	opened	closed

Save

  


No galvanic Connection to
the input U_e

 7.1 Components of A/D-Converters


Sample & Hold Circuit

Droop (Regeldifferenz):
Discharge of the Capacitance
because of leakage currents in
Q1 und IC2
(~1mV/ms)



Opening the relais

 Response time and
charging the Capacitance
(low pass from Q1 and C)



C should have a high value so that the „Droop“ is minimized
C should have a low value, so that fast changing signals can be followed


7.1 Components of A/D-Converters

N-Digits digital number

	2-digits number <hr/> Z ₁ Z ₀	N-digits number <hr/> Z _{N-1} ... Z ₁ Z ₀
Number of Digits	2	N
Number of Output Stages	4=2 ²	n= 2 ^N
Number of counting steps	3 = 2 ² -1	2 ^N -1
Quantisation step	$U_q = \frac{U_{e,\max}}{2^2 - 1}$	$U_q = \frac{U_{e,\max}}{2^N - 1}$
Shift Thresholds at	$U_{Um} = \frac{1}{2} \cdot \frac{U_{e,\max}}{2^2 - 1} + U_q + \dots + U_q$	$U_{Um} = \frac{1}{2} \cdot \frac{U_{e,\max}}{2^N - 1} + U_q + \dots + U_q$
Quantisation noise	$\frac{U_{e,\max}}{6} = \frac{1}{2} \cdot \frac{U_{e,\max}}{2^2 - 1}$	$\frac{1}{2} \cdot \frac{U_{e,\max}}{2^N - 1}$

7.1 Components of A/D-Converters

Quantisierungsfehler

 

$$|\text{error}_{\text{quantisierung}}| = \frac{\Delta X_{\text{LSB}}}{2} = \frac{1}{2} \cdot \frac{X_{\text{max}} - X_{\text{min}}}{\text{OutputSteps}}$$

$$= \frac{1}{2} \frac{X_{\text{max}} - X_{\text{min}}}{2^N - 1}$$

$X_{\text{max}} - X_{\text{min}}$: Analog values sector

N : Number of Digits


Signal-Noise-ratio

$$\frac{S}{N} [\text{dB}] = 20 \lg \left(\frac{U_{\text{signal,eff}}}{U_{\text{noise,eff}}} \right)$$

$$U_{\text{noise,eff}} = \sqrt{\frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} \left(U_{\text{LSB}} \frac{t}{T} \right)^2 dt} = \frac{U_{\text{LSB}}}{\sqrt{12}}$$

 7.2 Components of A/D-Converters

Classification of Analog/Digital-Converters



See: <http://groups.uni-paderborn.de/cc/arbeitsgebiete/messtech/simulationen/ad/index.html>


7.2 Flash A/D-Converter

Principle


Comparison of the voltage to be converted with well known graduated reference voltages

Properties

 - Resolution 4 to 12 Bit
- Suitable for a high signal dynamic



7.2 Flash A/D-Converter

 

Example: Parallel-A/D-Converter with 4-Comparators

Voltage	Comparator Signals	Digital Number	Output
	$K_1 \ K_2 \ K_3 \ K_4$	$\overline{z_2 z_1 z_0}$	U_E / U_{ref}
$0 \leq U_E < \frac{1}{4}U_0$	0 0 0 0	000	0
$\frac{1}{4}U_0 \leq U_E < \frac{2}{4}U_0$	1 0 0 0	001	0,25
$\frac{2}{4}U_0 \leq U_E < \frac{3}{4}U_0$	1 1 0 0	010	0,5
$\frac{3}{4}U_0 \leq U_E < \frac{4}{4}U_0$	1 1 1 0	011	0,75
$U_E \geq U_0$	1 1 1 1	100	1

Decoder


Conversion Time dependent on switching speed of the comparators and the coder

- 10^8 Values/sec
- high expenditure, 8-Bit ADU necessitates $2^8 - 1$ comparators!

 7.3 Iterative AD-Converter

Counting Procedure → Use of D/A-Converter


Advantage: better resolution through more adjustable steps



- Count increases by 1 $\rightarrow U_V$ increases by $Q = \Delta U$
- Reference voltage U_V at the output of the DAU
- Compare with U_e
- Equality \rightarrow stop counting
- otherwise the counter increased (at clock)
- new counter signal is D/A-converted
- Procedure is repeated until $U_V > U_e$

Conversion time is dependent on :

 
- Transient behavior of D/A-Converter
- Switching speed of comparators
- Input value
- Number of digits n of output(max. 2^n steps)
- Clock Frequency f



 
7.3 Iterative AD-Converter

Incremental Follow-Up-Converter

- forward and reverse counter
- By a new conversion U_v is not reset to „0“
- Saves time in comparison with the incremental converter



 The conversion is terminated, when U_v is alternating increased and decreased by ΔU




7.3 Iterative AD-Converter

Digital-Analog-Converter by Pulse Width Modulation

Basic Components

- Digital stream
- RC-low pass filter

 


Function


- The digital pulses have the same frequency
- The pulse width („High“-Duration) is proportional to the output voltage
- The digital pulse stream is low pass filtered
- The analog output voltage of the low pass filter is proportional to the mean duration of the „High“-level

7.4 A/D-Converter with an Intermediate Quantity

u/f-Converter

 


u/t-Converter

 

7.4 A/D-Converter with an Intermediate Quantity

Periode Duration Measurement

 


$$T_x = \frac{N_x}{f_0}$$

$$N_x = \frac{T_x}{T_0} = f_0 \cdot T_x$$

$$\left| \frac{\Delta T_x}{T_x} \right| = \left| \frac{\Delta N_x}{N_x} \right| + \left| \frac{\Delta f_0}{f_0} \right| \approx \left| \frac{1}{N_x} \right|$$

Frequency Measurement

 

$$f_x = \frac{N_x}{T_0}$$

$$\left| \frac{\Delta f_x}{f_x} \right| = \left| \frac{\Delta N_x}{N_x} \right| + \left| \frac{\Delta T_0}{T_0} \right| \approx \left| \frac{1}{N_x} \right|$$

7.4 A/D-Converter with an Intermediate Quantity u/f- Sawtooth-Converter

$$t_1 < t < t_x$$

$$U_a(t) = U_o - \frac{1}{C} \int_{t_1}^{t_x} \frac{U_x}{R} dt = U_o - \frac{1}{RC} \int_{t_1}^{t_x} U_x dt$$


If U_a reaches $U_r \rightarrow$ the relais is closed during T_a

The capacitance is discharged during the constant time T_a

$$f_x = \frac{1}{(t_x - t_1) + T_a}$$

The frequency of occurrence of the pulses is dependent on the Integration time ($t_x - t_1$)

 - Relative slow, sampling time can be until $2n / f_{ref}$ long
- Sensitive to noise-peaks



7.4 A/D-Converter with an Intermediate Quantity u/f- Converter by the charge balancing method

I_0 : Constant current source

$t < t_0$ u_x is integrated
Integration time is dependent on u_x



$t = t_0$ $U_a = U_r$

mono-stable trigger circuit changes ist input during T_a

Integration during T_a
(constant time interval)

T_g and f_g are the maesure for the voltage U_x

  Discharging during current source is connected
→ Faster conversion



7.4 A/D-Converter with an Intermediate Quantity

u/t- Pulse Wide Converter

$$U_a = U_{a,\max} - \frac{1}{RC} \int_0^t U_0 \cdot dt = U_{a,\max} - \frac{U_0 \cdot t}{RC}$$


$$U_a(t_3) = 0$$

$$U_a(t_x) = U_x$$


$$= U_{a,\max} - \frac{U_0 \cdot t_x}{RC} = \frac{U_0}{RC} (t_3 - t_x)$$

$$(t_3 - t_x) = \frac{U_x \cdot RC}{U_0} = \frac{N_x}{f}$$

$$U_x = \frac{U_0}{RC} \frac{N_x}{f}$$


 


 7.4 A/D-Converter with an Intermediate Quantity Dual Slope Voltage-Time -Converter




- First, U_e is integrated during the given Time intervall T_1 , than U_a is desintgrated through Integration of $-U_{ref}$ by 0
- Is $U_a=0$ reached, the counting is stopped
- The time intervall T_1 is well known but independent on U_e
- The time intervall T_2 of the desintegration is proportional to U_e

  7.4 A/D-Converter with an Intermediate Quantity Dual Slope Voltage-Time -Converter



 7.4 A/D-Converter with an Intermediate Quantity Dual Slope Voltage Time Converter



- Very high resolution
- Slow (typ. f_{Tast} a few 10 Hz)
- Not sensitive to drift (clock, RC,...) and to noise (because of integration)

$$U_a(t_3) = -\frac{1}{RC} \left[\int_{t_1}^{t_2} u_x dt - \int_{t_2}^{t_3} U_{ref} dt \right] = 0$$



$$u_x = U_{ref} \frac{N_2}{N_1}$$



$$\Rightarrow u_x(t_2 - t_1) - U_{ref}(t_3 - t_2) = 0$$

The precision is only dependent on U_{ref} !


$$\Rightarrow u_x N_1 - U_{ref} N_2 = 0$$

7.5 Sigma-Delta-Converter

1 Bit-Delta-Modulator

  


 1 Bit-Sigma-Delta-Modulator (Smoothed Version of the Delta-Modulator)



7.5 Sigma-Delta-Converter

Components

 

Properties

- Sampling frequency typ. 100 kHz
Oversampling: $f_a \gg f_{smax}$
- Typ. 10-24 Bit resolution
- Application in audio technology

7.5 Sigma-Delta-Converter

Possible Realisation


$$U_a > 0 \quad K = -1 \quad I_r = +I_0$$

$$U_a \leq 0 \quad K = +1 \quad I_r = -I_0$$


$$U_a = -\frac{1}{C} (i_x + i_r) \cdot T_0$$

$$U_x = \frac{N_1}{N_2} U_M = \frac{4}{5} \cdot 1V = 0,8V$$

 
Typical: Conversion Time 1 ms
 Resolution: >16 bit



7.5 Sigma-Delta-Converter

 


7.5 Sigma-Delta-Converter

 

 7.5 Sigma-Delta-Converter

Digital Decimation from Bit Stream



(Down Sampling, reducing the number of samples in a discrete-time signal)




Mean Value of the bit stream corresponds to:
Input signal **overlapped with disturbing signals**

The more bit stream pulses are used the more precise is the mean value
→ Oversampling is necessary


7.5 Sigma-Delta-Converter

  


7.5 Sigma-Delta-Converter

 

Comparator

 

Bit Stream


 


Low Pass Filtered Signal


$$F(s) = \frac{\omega_g}{s + \omega_g}$$

Digital Low Pass Filter:
  
$$U(t) = U_{ref} \cdot \frac{N_1}{N_{gesamt}}$$



7.5 Sigma-Delta-Converter

 


Example. Window 1


$$0.96 = 1 \cdot \frac{120}{125}$$

 Example. Window 2


$$0.75 = 1 \cdot \frac{94}{125}$$

The bigger the window is, the smaller the limit frequency of the digital Low Pass
 → Mean Value
 → Phase Shift



 


High Signal Value

 

Frequency of the disturbing signals in the neighborhood of the signal frequency P. 7-40


7.5 Sigma-Delta-Converter

1. Ordnung

 

Sigma-Delta-Converter 2. Order → Reducing disturbing signals

Not one after the other!

 

- Signal band width can be higher
- Clock rate kann be smaller
- Accuracy of the output signal can be higher (less conversion noise)

http://www.beis.de/Elektronik/DeltaSigma/DeltaSigma_D.html


7.5 Sigma-Delta-Converter

Structure

Two Disturbations

- Quantisation noise (Digitalisation)
- Conversion Noise (within the Bitstream) dependent on:
 - Order of the Sigma-Delta-Converter
 - Oversampling rate

 
7.5 Sigma-Delta-Converter Conversion Noise



Typical:

24 Bit, Modulator third order with 64-Times Oversampling
(-160 dB Conversion Noise and -147 dB Quantisation Noise)

7.5 Sigma-Delta-Converter

 


High Frequency


- Signal is supressed
- Distrubing Effects are amplified
("Alias-Effekt")

7.6 errors by A/D-Converter


Offset-Error

 


Integral Nonlinearity

 

Amplification Error

 

Differential Nonlinearity

 

Absolute Deviation of the width of the Quantisation Steps from Ideal Value 1 U_{LSB}

Overview A/D-Converter

	Flash Converter	Successive Approximation	Dual Slope	Sigma Delta
Main Advantages	Ultra-High Speed when power consumption not primary concern	Medium to high resolution (8 to 16bit), 5Msps and under, low power, small size.	high resolution, low power consumption, good noise performance	High resolution, low to medium speed, digital filter reduces anti-aliasing requirements.
Disadvantages	Metastability, high power consumption, large size, expensive.	Speed limited to ~5Msps. May require anti-aliasing filter.	Slow Conversion rate. High precision external components necessary	Higher order (4th order or higher) - multibit ADC and multibit feedback DAC.
Conversion Time	Ca. 10 ns-100ns Does not change with increased resolution.	Ca. 1 μ s-100 μ s Increases linearly with increased resolution.	Ca. x ms Increases linearly with increased resolution.	Ca. 200 μ s-2ms Tradeoff between data output rate and noise free resolution.
Typ. Resolution	4 bit 8 bit	8 bit 18 bit	12 bit 22 bit	16 bit 24 bit More bits?